

*Instructions:* This is a closed book, closed note exam. Calculators are not permitted. If you have a question, raise your hand and I will come to you. Please work the exam in pencil and do not separate the pages of the exam. For maximum credit, show your work.

*Good Luck!*

Your Name (*please print*) \_\_\_\_\_

1	2	3	4	5	total
<input type="text"/>					
32	34	18	34	34	152



Problem 1 (4 parts, 32 points)

Implementation Bonanza

For each part implement the specified device. **Label all inputs and outputs.**

Part A (8 points) Implement the expression below using N and P type switches.

$$OUT_x = \bar{A} \cdot B \cdot (\bar{C} + D) + \bar{E}$$

Part B (8 points) Implement the expression in mixed logic notation using NOR gates.

$$OUT_y = (A + \overline{B + C}) \cdot \bar{D}$$

Part C (8 points) Implement a 1 to 4 DEMUX using only pass gates and inverters.

Part D (8 points) Implement a full adder using AND, OR, NAND, NOR, NOT, &amp; XOR gates.

## Problem 2 (2 parts, 34 points)

Even Average

In this problem, you will write a subroutine that determines the average of even numbers in a variable length array in memory. **Comments for each instruction and labels are already provided.** Input parameters to this subroutine include a pointer to the first array element (\$1) and the number of elements in the array (\$2). The result (the average of even numbers) is returned in \$3. As always, the return address for this subroutine arrives in \$31.

input parameters				result		working registers					
reg	content	reg	content	reg	content	reg	content	reg	content	reg	content
\$1	array pointer	\$2	# array elements	\$3	input / result	\$4	running sum	\$5	# even values	\$6	predicate

Part A (24 points) Write a subroutine that computes the average of even values in an array.

label	instruction	comment
EvenAvg:		# clear running sum
		# clear # of even values
		# adjust # elem for byte address
		# point to addr after last elem
Loop:		# load next array element
		# test if even or odd
		# if odd, skip
		# if even, add to running sum
		# and increment # even values
Skip:		# adjust array ptr to next elem
		# if not at end of array, loop
		# compute even average
		# return to caller

Part B (10 points) Write a code fragment that calls EvenAvg for a 100 element array starting at address 5000. When the subroutine completes, store the result at memory location 6000.

label	instruction	comment
		# load array starting pointer
		# load array size (# elements)
		# call even array average
		# load address for result
		# store result to memory

Problem 3 (2 parts, 18 points)

Instruction Formats

Part A (9 points) Consider the instruction set architecture below with fields containing zeros.

000 0000	0 0000 0000	0 0000 0000	00 0000 0000 0000 0000
opcode	dest. reg.	source 1 reg.	immediate value

What is the maximum number of opcodes? \_\_\_\_\_

What is the number of registers? \_\_\_\_\_

What is the range of the signed immediate value? \_\_\_\_\_

Part B (9 points) List three differences between a branch and a jump in the MIPS ISA.

1: \_\_\_\_\_

2: \_\_\_\_\_

3: \_\_\_\_\_

Problem 4 (4 parts, 34 points)

State of the Union

Part A (7 points) Implement an RS latch with active high inputs, R and S. Use only basic gates (AND, OR, NAND, NOR, and NOT). Label the inputs and output. Also complete the behavior table. Note -Out means  $\overline{Out}$ .

R ———

S ———

——— Out

———  $\overline{Out}$

R	S	Out	-Out
0	0		
1	0		
0	1		
1	1		

Part B (7 points) Expand the RS latch to a transparent latch and complete the truth table. Use only basic gates (AND, OR, NAND, NOR, and NOT). Label the inputs and output. Also complete the behavior table.


In ———

——— Out

———  $\overline{Out}$


In	En	Out	-Out
A	0		
A	1		

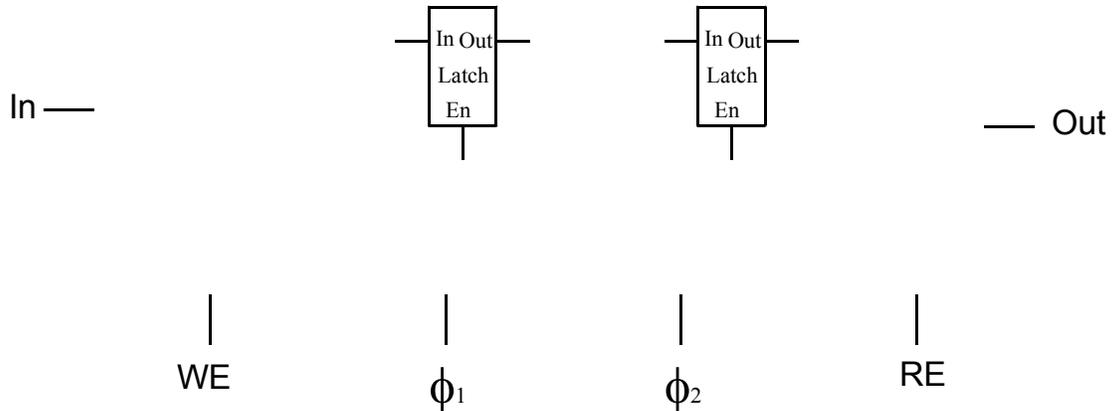Part C (12 points) Build a register using two transparent latches plus a 2to1 mux (draw the labeled icon), a pass gate, and an inverter. Again, complete the behavior table. Recall that the CLK signal indicates a full  $\Phi_1 \Phi_2$  cycle; so the output should be the value at the end of a cycle (with the given inputs).



In	WE	RE	Clk	Out
A	0	0	↑↓	
A	1	0	↑↓	
A	0	1	↑↓	
A	1	1	↑↓	

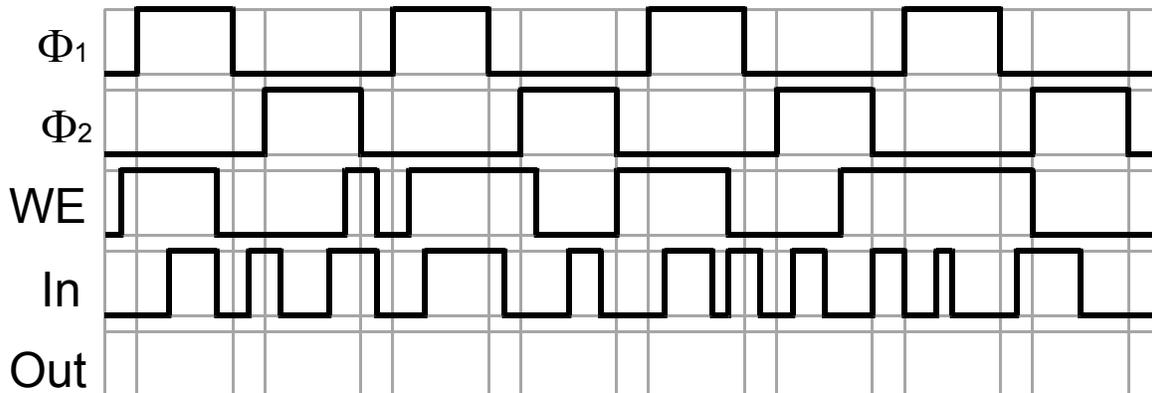Part D (8 points) Assume the following signals are applied to your register. Draw the output signal **Out**. Draw a vertical line where **In** is sampled. Draw *crosshatch* where **Out** is unknown.



Problem 5 (3 parts, 34 points)

This and That

Part A (12 points) For the following Karnaugh Map, derive a simplified *product of sums* expression. Circle and list the prime implicants, indicating which are essential.

	$\bar{B}$	$B$			
$\bar{A}$	0	0	1	1	$\bar{C}$
$A$	1	0	0	1	$C$
	$\bar{D}$	$D$	$\bar{D}$		

prime implicants		essential?		
		yes	no	
		<input type="checkbox"/>	<input type="checkbox"/>	
		<input type="checkbox"/>	<input type="checkbox"/>	
		<input type="checkbox"/>	<input type="checkbox"/>	
		<input type="checkbox"/>	<input type="checkbox"/>	
		<input type="checkbox"/>	<input type="checkbox"/>	
		<input type="checkbox"/>	<input type="checkbox"/>	
		<input type="checkbox"/>	<input type="checkbox"/>	

simplified POS expression \_\_\_\_\_


Part B (12 points) Using the supplied datapath, write a microcode fragment to accomplish the following expression. Express all values in hexadecimal notation. Use 'X' when a value is don't cared. For maximum credit, complete the description field.  $\cap$  means bitwise logical AND.

$$R_1 = \left( \frac{mem[100]}{256} \cap 255 \right)$$

#	X	Y	Z	rwe	im en	im va	au en	-a /s	lu en	lf	su en	st	ld en	st en	r/-w	msel	description
1																	
2																	
3																	
4																	

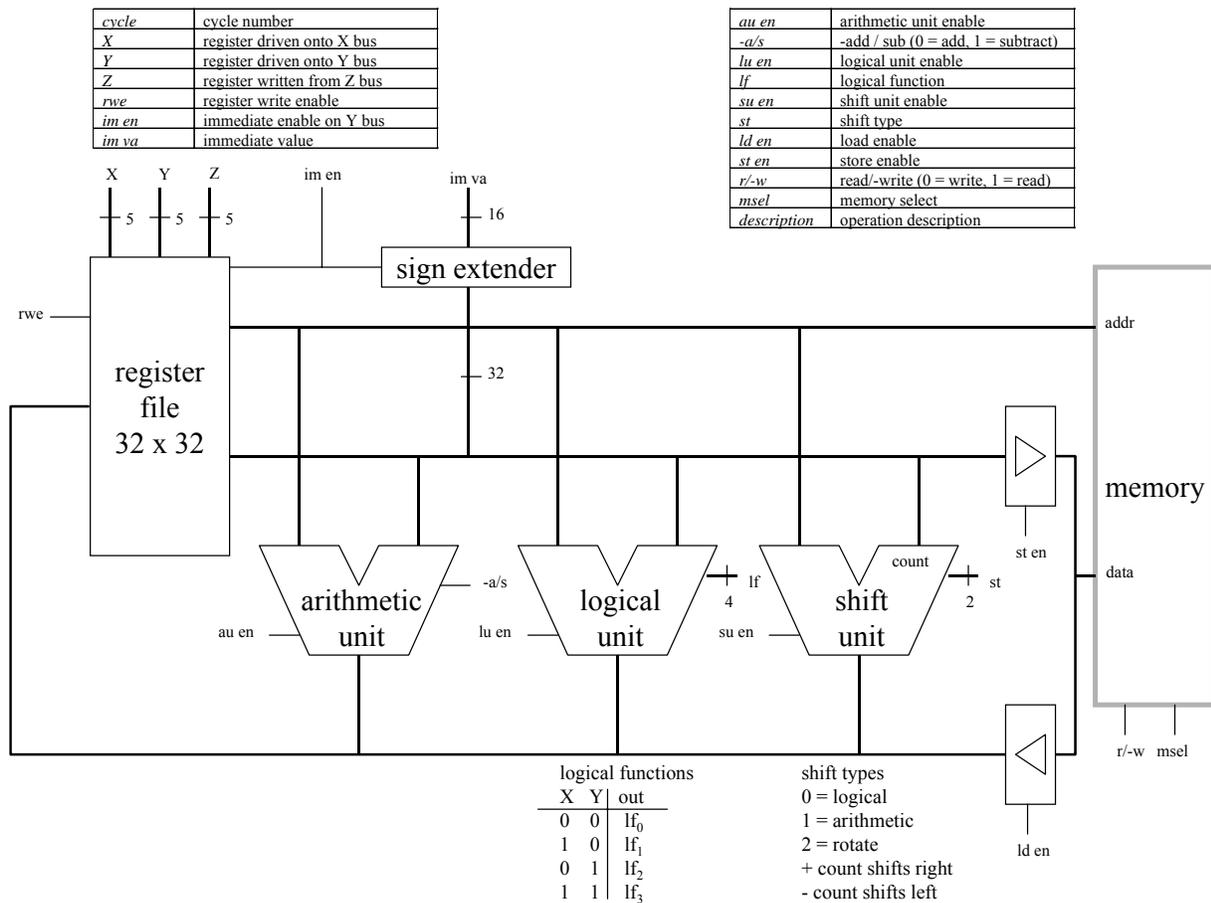Part C (10 points) Consider a **4 Gbyte** memory system with **512 million** addresses of **8 byte words** using **1 Gbit** DRAM chips organized as **64 million** addresses by **16 bit words**.

- word address lines for memory system \_\_\_\_\_
- chips needed in one bank \_\_\_\_\_
- banks for memory system \_\_\_\_\_
- memory decoder required ( $n$  to  $m$ ) \_\_\_\_\_
- DRAM chips required \_\_\_\_\_



instruction	example	meaning
add	add \$1,\$2,\$3	\$1 = \$2 + \$3
subtract	sub \$1,\$2,\$3	\$1 = \$2 - \$3
add immediate	addi \$1,\$2,100	\$1 = \$2 + 100
multiply	mul \$1,\$2,\$3	\$1 = \$2 * \$3
divide	div \$1,\$2,\$3	\$1 = \$2 / \$3
and	and \$1,\$2,\$3	\$1 = \$2 & \$3
or	or \$1,\$2,\$3	\$1 = \$2   \$3
xor	xor \$1,\$2,\$3	\$1 = \$2 xor \$3
and immediate	andi \$1,\$2,100	\$1 = \$2 & 100
or immediate	ori \$1,\$2,100	\$1 = \$2   100
xor immediate	xori \$1,\$2,100	\$1 = \$2 xor 100
shift left logical	sll \$1,\$2,5	\$1 = \$2 << 5 (logical)
shift right logical	srl \$1,\$2,5	\$1 = \$2 >> 5 (logical)
shift left arithmetic	sla \$1,\$2,5	\$1 = \$2 << 5 (arithmetic)
shift right arithmetic	sra \$1,\$2,5	\$1 = \$2 >> 5 (arithmetic)
load word	lw \$1, (\$2)	\$1 = memory [\$2]
store word	sw \$1, (\$2)	memory [\$2] = \$1
load upper immediate	lui \$1,100	\$1 = 100 x 2 <sup>16</sup>
branch if equal	beq \$1,\$2,100	if (\$1 = \$2), PC = PC + 4 + (100*4)
branch if not equal	bne \$1,\$2,100	if (\$1 ≠ \$2), PC = PC + 4 + (100*4)
set if less than	slt \$1, \$2, \$3	if (\$2 < \$3), \$1 = 1 else \$1 = 0
set if less than immediate	slti \$1, \$2, 100	if (\$2 < 100), \$1 = 1 else \$1 = 0
jump	j 10000	PC = 10000
jump register	jr \$31	PC = \$31
jump and link	jal 10000	\$31 = PC + 4; PC = 10000