



Problem 1 (3 parts, 24 points)

Design This

Complete each design below. Be sure to label all signals.

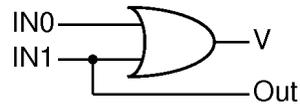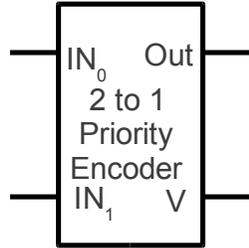Part A: Define a 2 to 1 priority encoder, where  $I_1 > I_0$ , by completing the behavior table.


Implement the 2 to 1 encoder using **one** basic gate. Only true (non-complemented) inputs are available. Label all inputs (IN0, IN1) and outputs (Out, V).



IN <sub>0</sub>	IN <sub>1</sub>	V	Out
0	0	0	X
1	0	1	0
X	1	1	1

Part B: Implement a 1 to 2 demux using only pass gates and an inverter. Determine # of switches needed.

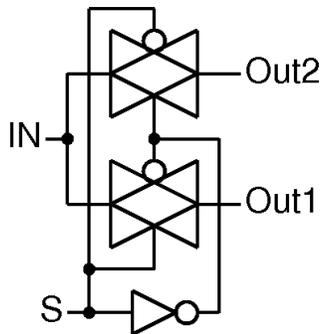Part C: Complete the truth table for even parity. Then write a sum of products (SOP) expression.



A	B	Out
0	0	1
1	0	0
0	1	0
1	1	1

# switches = 3 x 2 = 6T


$\overline{A \oplus B} = \underline{\overline{A} \cdot \overline{B} + A \cdot B}$

Problem 2 (4 parts, 32 points)

Design That

Complete each design below. Be sure to label all signals.

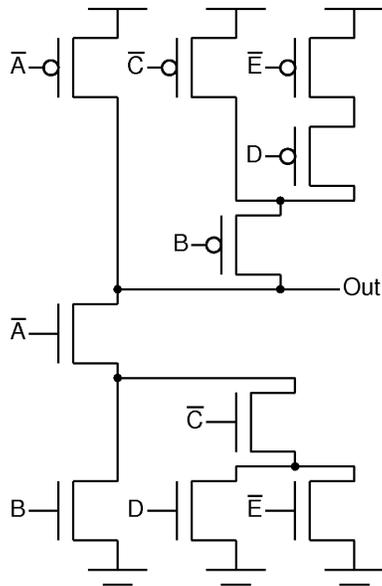
Part A: Complete the following CMOS design. Also express its behavior.



Out =  $A + \bar{B} \cdot (C + \bar{D} \cdot E)$

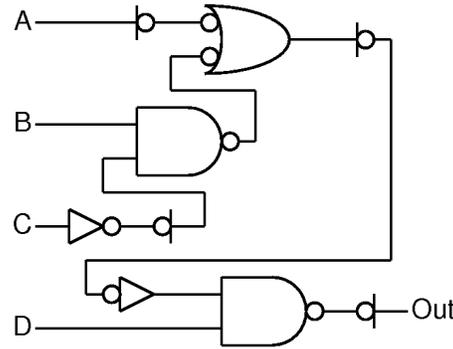
Part B: Implement the following expression using NAND and NOT gates. Use proper mixed logic design. Determine # of switches needed.

Out =  $\bar{\bar{A}} + B \cdot \bar{C} \cdot D$




# switches =  $3 \times 4 + 2 \times 2 = 16T$

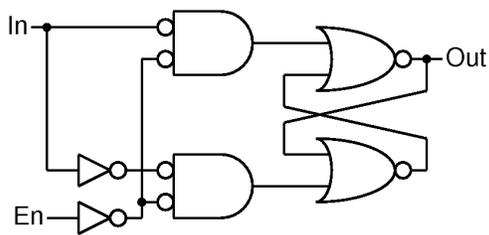Part C: Implement a transparent latch using only NOR and NOT gates.



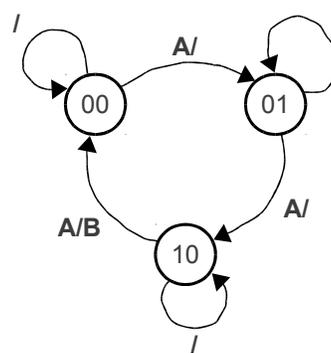Part D: Draw the state table for the following state diagram.




A	S <sub>1</sub>	S <sub>0</sub>	NS <sub>1</sub>	NS <sub>0</sub>	B
0	0	0	0	0	0
1	0	0	0	1	0
0	0	1	0	1	0
1	0	1	1	0	0
0	1	0	1	0	0
1	1	0	0	0	1

Problem 3 (3 parts, 30 points)


Accountable

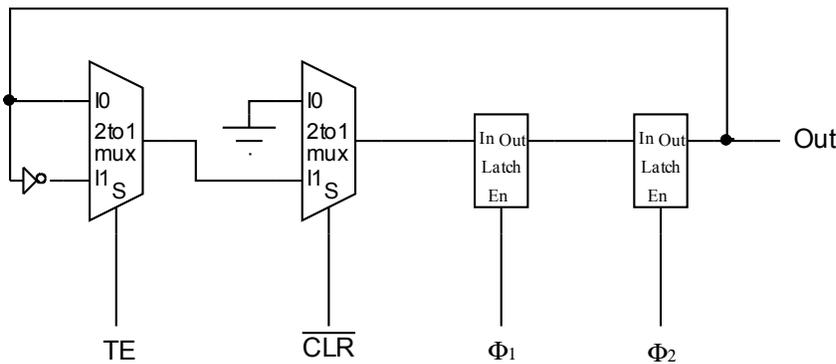Part A (10 points) Design a toggle cell using **transparent latches**, **2to1 muxes**, and **inverters** (use icons, **labeling inputs & outputs**). Your toggle cell should have an active high toggle enable input **TE**, and an active low clear input **CLR**, clock inputs  $\Phi_1$  and  $\Phi_2$ , and an output **Out**. The **CLR** signal has precedence over **TE**. Also complete the behavior table for the toggle cell.




TE	$\overline{\text{CLR}}$	CLK	Out
0	0	↑↓	0
1	0	↑↓	0
0	1	↑↓	$Q_0$
1	1	↑↓	$\overline{Q_0}$

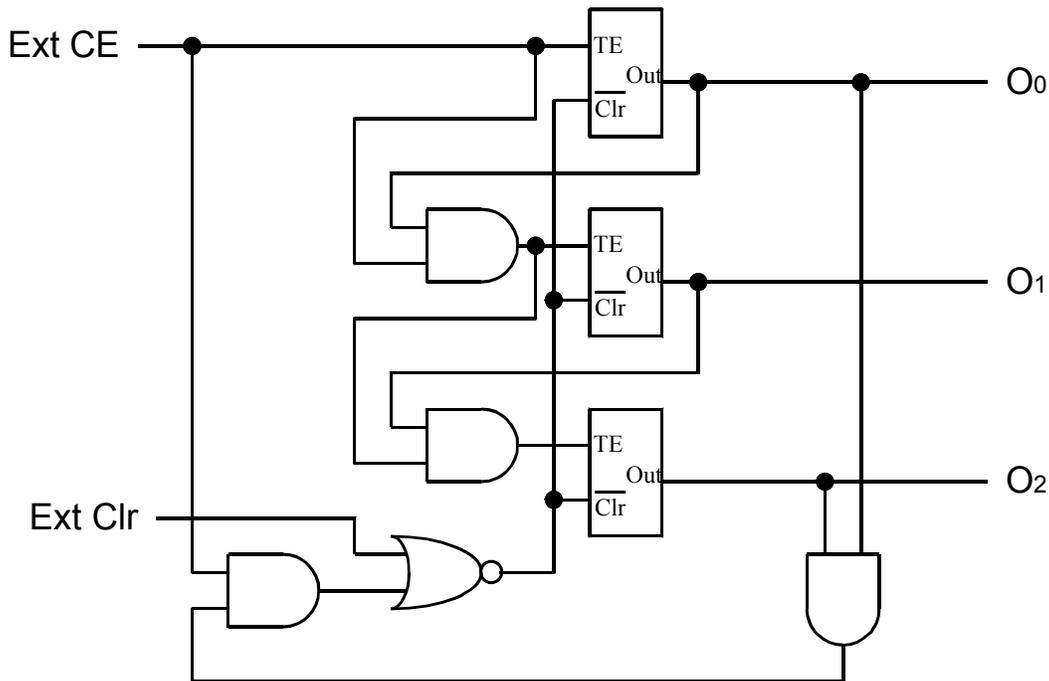Part B (10 points) Now combine these toggle cells to build a **divide by 6** counter. Your counter should have an external clear, external count enable, and three count outputs  $O_2$ ,  $O_1$ ,  $O_0$ . Use any basic gates (AND, OR, NAND, NOR, & NOT) you require. Assume clock inputs to the toggle cells are already connected. *Your design should support multi-digit systems.*



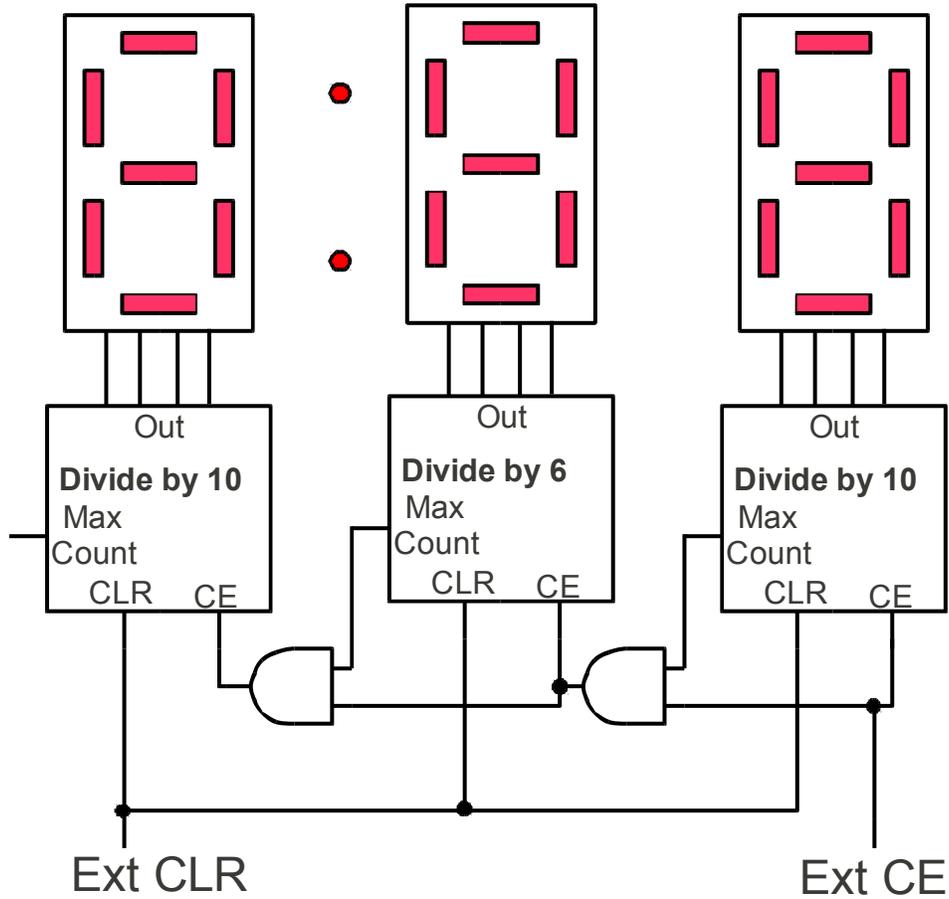Part C (10 points) Build a stopwatch that counts seconds and minutes using divide by N counters drawn below. **Be sure to fill in the needed divider for seconds, tens of seconds, and minutes.** Use any basic gates you require. Assume a one hertz clock is already connected.



Problem 4 (2 parts, 48 points)

Microcode in Reverse

Part A (20 points) Translate this undocumented microcode fragment (in hexadecimal) to corresponding MIPS assembly instructions. Also include comments summarizing the instruction.

#	X	Y	Z	rwe	im en	im va	au en	- a/s	lu en	lf	su en	st	ld en	st en	r/-w	msel
1	5	0	7	1	0	0	0	0	0	0	0	0	1	0	1	1
2	7	0	9	1	1	C	0	0	0	0	1	0	0	0	0	0
3	9	0	9	1	1	FFF	0	0	1	8	0	0	0	0	0	0
4	9	A	A	1	0	0	1	0	0	0	0	0	0	0	0	0
5	8	A	0	0	0	0	0	0	0	0	0	0	0	1	0	1

1	lw	\$7, 0(\$5)	# \$7 ← mem[pointer \$5]
2	srl	\$9, \$7, 12	# \$9 ← \$7 >> 12
3	andi	\$9, \$9, 0xFFF	# \$9 ← \$9 & 0xFFF
4	add	\$10, \$9, \$10	# \$10 ← \$10 + \$9
5	sw	\$10, 0(\$8)	# mem[pointer \$8] ← \$10

Part B (28 points) Complete a recursive subroutine that computes the factorial of N. Assume N is received in \$1 and N! is returned in \$2. \$29 is the stack pointer.

label	instruction	comment
Fact:	addi \$02, \$00, 1	# init result to 1
	slti \$03, \$01, 2	# if N < 2
	bne \$03, \$00, Done	# you're done
	addi \$29, \$29, -8	# allocate stack space
	sw \$31, 4(\$29)	# push return address
	sw \$01, 0(\$29)	# push N
	addi \$01, \$01, -1	# decrement N
	jal Fact	# call Fact(N-1)
	lw \$01, 0(\$29)	# pop N
	lw \$31, 4(\$29)	# pop return address
	addi \$29, \$29, 8	# deallocate stack space
	mult \$01, \$02	# N * Fact(N-1)
	mflo \$2	# place result in \$2
Done:	jr \$31	# return to caller

Problem 5 (4 parts, 39 points)

“Random Bits”

Part A (9 points) Consider the instruction set architecture below with fields containing zeros.

0 0000	0000	0000	0000 0000 0000 0000 0000
opcode	dest. reg.	source 1 reg.	immediate value

- What is the maximum number of opcodes?  $2^5 = 32$
- What is the number of registers?  $2^4 = 16$
- What is the range of the signed immediate value?  $2^{20} = \pm 512K$

Part B (9 points) For the representations below, determine the most positive value and the step size (difference between sequential values). **All answers should be expressed in decimal notation.** Fractions (e.g., 3/16ths) may be used. Signed representations are two’s complement.

representation	most positive value	step size
signed integer (15 bits) . (0 bits)	$2^{15} = 16K$	1
unsigned fixed-point (10 bits) . (5 bits)	$2^{10} = 1024 \approx 1K$	1/32
signed fixed-point (5 bits) . (10 bits)	15 999/1000	1/1K = .001

Part C (9 points) A 16 bit floating point representation has a 10 bit mantissa field, a 5 bit exponent field, and one sign bit. *Express all answers in decimal.* Fractions (e.g., 3/8) are okay.

- What is the largest value that can be represented (closest to infinity)?  $32K$
- What is the smallest value that can be represented (closest to zero)?  $1/64K$
- How many decimal significant figures are supported?  $3$

Part D (12 points) For each problem below, compute the operations using the rules of arithmetic, and indicate whether an overflow occurs assuming all numbers are expressed using a **five bit unsigned fixed-point** and **five bit two’s complement fixed-point** representations.

	11.1	11.011	10101	100.00
	+ 111.1	+ 10.101	- 1010	+ .01
result	1011.0	10.000	1011	100.01

unsigned error?	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes	<input type="checkbox"/> no <input checked="" type="checkbox"/> yes	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes
signed error?	<input type="checkbox"/> no <input checked="" type="checkbox"/> yes	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes	<input type="checkbox"/> no <input checked="" type="checkbox"/> yes	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes