

Instructions: This is a closed book, closed note exam. Calculators are not permitted. If you have a question, raise your hand and I will come to you. Please work the exam in pencil and do not separate the pages of the exam. For maximum credit, show your work.

Good Luck!

Your Name (*please print*) _____

1	2	3	4	total
<input type="text"/>				
24	28	24	24	100



Problem 2 (3 parts, 28 points)

Number Systems

Part A (10 points) Convert the following notations:

binary notation	decimal notation
1010 1010.	
0101 0101.1001	
1111 1111.1111	
octal notation	hexadecimal notation
5755.7	
33.33	

Part B (12 points) For the 24 bit representations below, determine the most positive value and the step size (difference between sequential values). **All answers should be expressed in decimal notation.** Fractions (e.g., 3/16ths) may be used. Signed representations are two's complement.

representation	most positive value	step size
unsigned integer (24 bits) . (0 bits)		
signed fixed-point (18 bits) . (6 bits)		
signed fixed-point (15 bits) . (9 bits)		
signed fixed-point (12 bits) . (12 bits)		

Part C (6 points) A 48 bit floating point representation has a 37 bit mantissa field, a 10 bit exponent field, and one sign bit.

What is the largest value that can be represented (closest to infinity)? 2 _____

What is the smallest value that can be represented (closest to zero)? 2 _____

How many decimal significant figures are supported? _____

Problem 3 (3 parts, 24 points)


“Math is easy”

Part A (12 points) For each problem below, compute the operations using the rules of arithmetic, and indicate whether an overflow occurs assuming all numbers are expressed using a **six bit unsigned fixed-point** and **six bit two’s complement fixed-point** representations.

111.010	11.111	100.000	10.101
$+ 111.011$	$+ 0.001$	$- 10.001$	$- 101.010$

result
unsigned error?
signed error?

 Part B (6 points) The adder below adds two four bit numbers A and B and produces a four bit result S. Add extra digital logic to support subtraction as well as addition. Label inputs $X_3, X_2, X_1, X_0, Y_3, Y_2, Y_1, Y_0, \overline{ADD}/SUB$ and outputs Z_3, Z_2, Z_1, Z_0 .



Part C (6 points) Write two Boolean expressions indicating signed two’s complement addition and subtraction overflow using inputs X_3, Y_3, Z_3 . These SOP expressions should be true when overflow occurs.

addition overflow = _____

subtraction overflow = _____

Problem 4 (3 parts, 24 points)

“Register your knowledge”


Part A (8 points) Implement a 2 to 1 multiplexer using only pass gates and inverters. Label all inputs (IN_0 , IN_1 , S) and output (Out).

Part B (10 points) Implement a register below using needed muxes, latches, pass gates, and inverters (all in icon form). Complete the behavior table at right. Recall that the CLK signal indicates a full $\Phi_1 \Phi_2$ cycle; so the output should be the value at the end of a cycle (with the given inputs).

In	WE	RE	Clk	Out
A	0	0	$\uparrow\downarrow$	
A	1	0	$\uparrow\downarrow$	
A	0	1	$\uparrow\downarrow$	
A	1	1	$\uparrow\downarrow$	

In —

— Out

 

Part C (6 points) Assume the following signals are applied to your register. Draw the output signal **Out**. Draw a vertical line where **In** is sampled. Draw *crosshatch* where **Out** is unknown.

