

Problem 1 (3 parts, 31 points)

Numbers of Reason

Part A (13 points) Convert the following notations:

binary notation	decimal notation
1 1100 1001.1001	457.5625
1 1111 0001	497
1 1001.11	25.75
binary notation	hexadecimal notation
101 1010 0101.0101 1010 101	5A5.5AA
1100 1010 0001 0001.1100 1010 1011	CA11.CAB

Part B (12 points) For the 25 bit representations below, determine the most positive value and the step size (difference between sequential values). **All answers should be expressed in decimal notation.** Fractions (e.g., 3/16ths) may be used. Signed representations are two's complement.

representation	most positive value	step size
unsigned fixed-point (20 bits) . (5 bits)	1M	1/32
signed integer (25 bits) . (0 bits)	16M	1
signed fixed-point (13 bits) . (12 bits)	4K	1/4K
signed fixed-point (9 bits) . (16 bits)	256	1/64K

Part C (6 points) A 25 bit floating point representation has a 17 bit mantissa field, a 7 bit exponent field, and one sign bit.

What is the largest value that can be represented (closest to infinity)? 2^{63}

What is the smallest value that can be represented (closest to zero)? 2^{-64}

How many decimal significant figures are supported? 5


Problem 2 (3 parts, 24 points)

“It doesn't add up”

Part A (12 points) For each problem below, compute the operations using the rules of arithmetic, and indicate whether an overflow occurs assuming all numbers are expressed using a **five bit unsigned fixed-point** and **five bit two's complement fixed-point** representations.

	11.1	1101.1	0.0	1010.1
	+ 111.1	+ 1100.1	-1000.1	- 101.0
result	1011.0	1010.0	0111.1	101.1
unsigned error?	<input type="checkbox"/> no <input type="checkbox"/> yes	<input type="checkbox"/> no <input checked="" type="checkbox"/> yes	<input type="checkbox"/> no <input checked="" type="checkbox"/> yes	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes
signed error?	<input type="checkbox"/> no <input checked="" type="checkbox"/> yes	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes	<input checked="" type="checkbox"/> no <input type="checkbox"/> yes	<input type="checkbox"/> no <input checked="" type="checkbox"/> yes

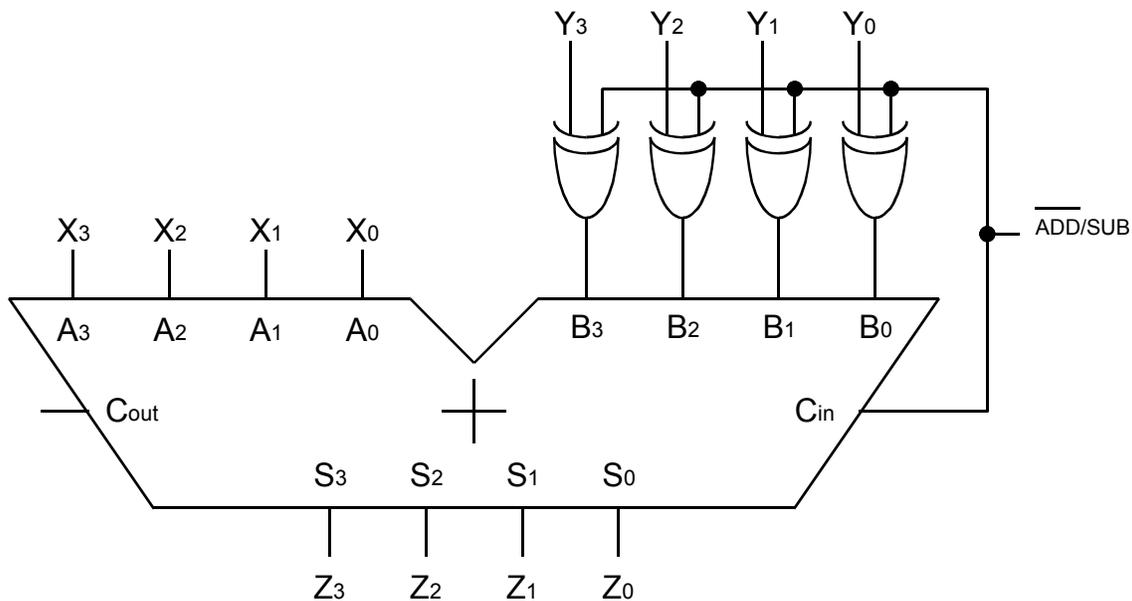Part B (6 points) The adder below adds two four bit numbers A and B and produces a four bit result S. Add extra digital logic to support subtraction as well as addition. Label inputs $X_3, X_2, X_1, X_0, Y_3, Y_2, Y_1, Y_0, \overline{ADD/SUB}$ and outputs Z_3, Z_2, Z_1, Z_0 .




Part C (6 points) Write two Boolean expressions indicating signed two's complement addition and subtraction overflow using inputs X_3, Y_3, Z_3 . These SOP expressions should be true when overflow occurs.

addition overflow = $X_3 Y_3 \bar{Z}_3 + \bar{X}_3 \bar{Y}_3 Z_3$

subtraction overflow = $X_3 \bar{Y}_3 \bar{Z}_3 + \bar{X}_3 Y_3 Z_3$


Problem 3 (3 parts, 24 points)
Part A (10 points) Implement a transparent latch using **only pass gates and inverters**.

Achieve a Happy State

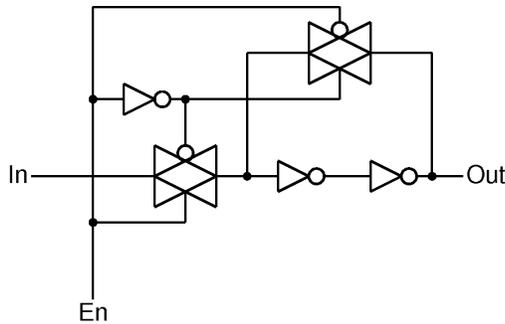

IN	EN	OUT	$\overline{\text{OUT}}$
A	0	Q_0	$\overline{Q_0}$
A	1	A	\overline{A}

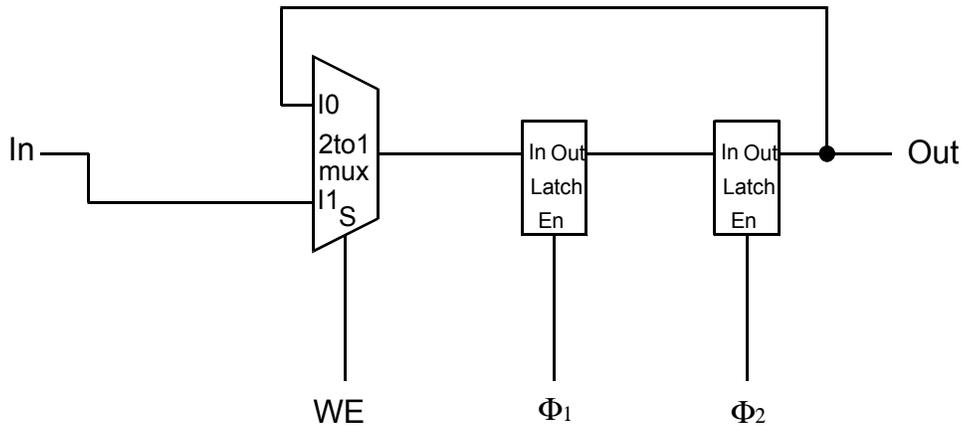Part B (8 points) Implement a one bit register with write enable using only the components drawn below. Label inputs **In**, write enable **WE**, clocks Φ_1 , and Φ_2 , and output **Out**.




Part C (6 points) Assume the following signals are applied to a register. Draw the output signal **Out**. Draw a vertical line where **In** is sampled. Draw crosshatch where **Out** is unknown.

Problem 4 (3 parts, 21 points)

“A chip off the old block”

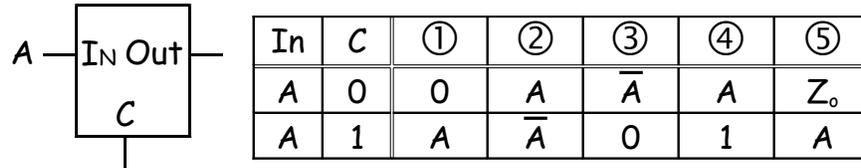
Part A (15 points) Consider the five definitions for the block drawn below. One block input is the logical value A . The other input is the control value C . The output behavior for each of the five definitions is given in the table. Complete the full truth table and state the *logical (gate) names* for each definition. (hint: the first block one appears to mask A when its control input is low.)



In	C	①	②	③	④	⑤
0	0	0	0	1	0	Z ₀
1	0	0	1	0	1	Z ₀
0	1	0	1	0	1	0
1	1	1	0	0	1	1

- | | | | | | |
|---|-----|---|-----------|---|-----|
| ① | AND | ② | XOR | ③ | NOR |
| ④ | OR | ⑤ | Pass Gate | | |

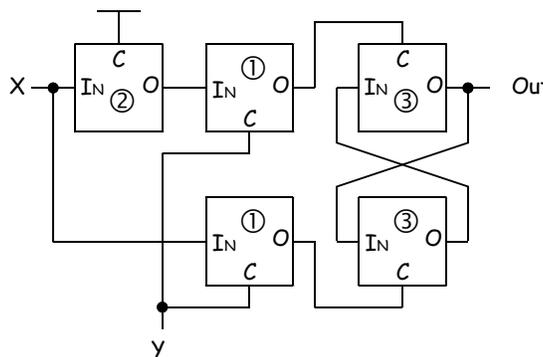Part B (6 points) The circuit below is built using these blocks. Describe its behavior. Also give the circuits common name.



X	y	Out
0	0	Q ₀
1	0	Q ₀
0	1	0
1	1	1

It's a transparent latch