

Instructions: This is a closed book, closed note exam. Calculators are not permitted. If you have a question, raise your hand and I will come to you. Please work the exam in pencil and do not separate the pages of the exam. For maximum credit, show your work.
Good Luck!

Your Name (*please print*) _____

1	2	3	4	total
<input type="text"/>				
30	26	26	18	100



Problem 1 (3 parts, 30 points)

Memory Systems

Part A (12 points) Consider a **1 Gbit** DRAM chip organized as **32 million addresses** of **32-bit words**. Assume both the DRAM cell and the DRAM chip are square. The column number and offset concatenate to form the memory address. Using the organization approach discussed in class, answer the following questions about the chip. *Express all answers in decimal (not powers of two).*

- total number of bits in address _____
- number of columns _____
- column decoder required (n to m) _____
- number of words per column _____
- type of mux required (n to m) _____
- number of address lines in column offset _____

Part B (10 points) Consider an **8 Gbyte** memory system with **1 billion addresses** of **64-bit words** using a **32 million address by 32-bit word** memory DRAM chip.

- word** address lines for memory system _____
- chips needed in one bank _____
- banks for memory system _____
- memory decoder required (n to m) _____
- DRAM chips required _____

Part C (8 points) Design a **16 million address by 4 bit** memory system with **4 million x 4** memory chips. *Label all busses and indicate bit width.* Assume R/W is connected and not shown here. Use a bank decoder if necessary. Be sure to include the address bus, data bus, and MSEL.

Problem 2 (3 parts, 26 points)

Datapath Elements

Part A (6 points) Suppose the following inputs (in hexadecimal) are applied to the 32-bit barrel shifter used in the datapath. Determine the output (in hexadecimal). Assume the shift amount is drawn from the 16-bit immediate value.

Shift Type	Shift Amount	Input Value	Output Value
arithmetic	0x0008	ABCD12EF	
rotate	0xFFF4	DEAF7892	
arithmetic	0xFFF0	FACE2537	

Part B (8 points) For each bitwise logical function specification below, determine the LF code (in hexadecimal) to correctly program the logical unit.

X	Y	Out	logical function	LF
0	0	LF ₀	$Y + X$	
1	0	LF ₁	X	
0	1	LF ₂	$X \oplus Y$	
1	1	LF ₃	$X \cdot Y$	

Part C (12 points) Given the following state table, draw the corresponding state diagram below.

S ₁	S ₀	H/M	NS ₁	NS ₀	Out	S ₁	S ₀	H/M	NS ₁	NS ₀	Out
0	0	0	0	1	0	1	0	0	0	0	1
0	0	1	0	0	0	1	0	1	0	0	0
0	1	0	1	0	0	1	1	0	x	x	x
0	1	1	0	0	0	1	1	1	x	x	x

Give the simplified Boolean expression for computing NS₁ in terms of the current state and the input.

NS₁ = _____.

Problem 3 (3 parts, 26 points)

Microcode

Using the supplied datapath, write microcode fragments to accomplish the following procedures. Express all values, except memory addresses, in hexadecimal notation. Use ‘X’ when a value is don’t cared. For maximum credit, complete the description field. **In each part, modify only registers 7 & 8.**

Part A (5 points)

$$R_7 = (R_8 - 12) / 128$$

#	X	Y	Z	rwe	im en	im va	au en	s/a	lu en	lf	su en	st	ld en	st en	r/w	mselect	description
1																	
2																	
3																	

Part B (15 points) Compute the logical OR of mem[4000] and R_3 and store the result in mem[4004] (that is, mem[4004] gets mem[4000]+ R_3 , where “+” is “logical or”).

#	X	Y	Z	rwe	im en	im va	au en	s/a	lu en	lf	su en	st	ld en	st en	r/w	mselect	description
1																	
2																	
3																	
4																	
5																	
6																	

Part C (6 points)

$$R_7 = 15 \cdot R_8 \quad (\text{multiply } R_8 \text{ by } 15)$$

#	X	Y	Z	rwe	im en	im va	au en	s/a	lu en	lf	su en	st	ld en	st en	r/w	mselect	description
1																	
2																	
3																	
4																	

Problem 4 (2 parts, 18 points)


Counters

Part A (8 points) Design a toggle cell using *only transparent latches and basic gates (XOR, AND, OR, NAND, NOR, NOT)*. Use an icon for the transparent latches. Your toggle cell should have an active high toggle enable input **TE**, and an active low clear input \overline{CLR} , clock inputs Φ_1 and Φ_2 , and an output **Out**. The \overline{CLR} signal has precedence over **TE**. Label all signals. Also complete the behavior table for the toggle cell.


TE	\overline{CLR}	CLK	Out
0	0	$\uparrow\downarrow$	
1	0	$\uparrow\downarrow$	
0	1	$\uparrow\downarrow$	
1	1	$\uparrow\downarrow$	

Part B (10 points) Now combine these toggle cells to build a **divide by thirteen** counter. Your counter should have an external clear, external count enable, and four count outputs O_3, O_2, O_1, O_0 . Use any basic gates (AND, OR, NAND, NOR, XOR & NOT) you require. Assume clock inputs to the toggle cells are already connected. Your design must support multi-digit systems.


Ext CE —

 

— O_0

 


— O_1

 

— O_2

Ext CLR —

 

— O_3

