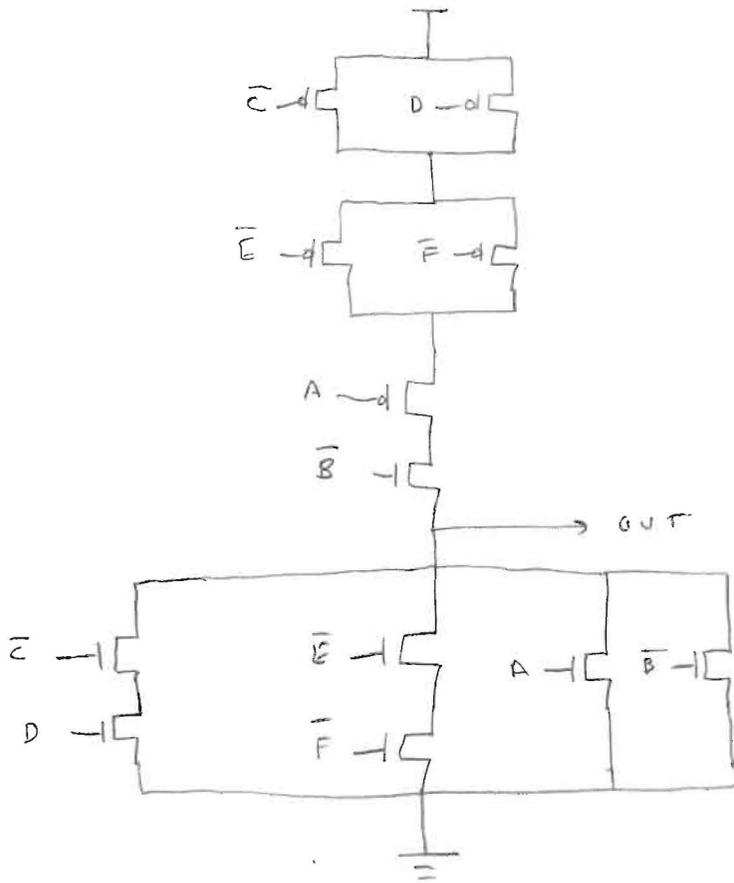


5 pages, 100 possible points. **Show your work for any possible partial credit.**

Switch level circuits:

1) (15 total point) For the expression below, create a switch level implementation using N and P type switches. Assume both inputs and their complements are available. Your design should contain no shorts or floats. Implement the equations exactly as they are (no simplifying).

$$\text{Out}_x = (C + \overline{D}) \cdot (E + F) \cdot \overline{A} \cdot B$$



Switch-Ready Expressions:

2) (15 points) Transform each of the following Boolean expressions to a form where they are ready for switch level implementation (i.e., there should only be bars over input variables, not over operations). The behavior of the expression should remain unchanged. **Do not implement**, just show the new Boolean equation without any "big bars".

$$\text{Outx} = \overline{(A + B)(C + D)(E + F)}$$


$$\overline{\overline{(A+B)} + \overline{(C+D)} + \overline{(E+F)}}$$

$$(A+B) + \overline{(C+D)} + (E+F)$$

$$(A+B) + \overline{\overline{(C \cdot D)}} + (E+F)$$

$$(A+B) + \overline{C} \cdot \overline{D} + (E+F)$$

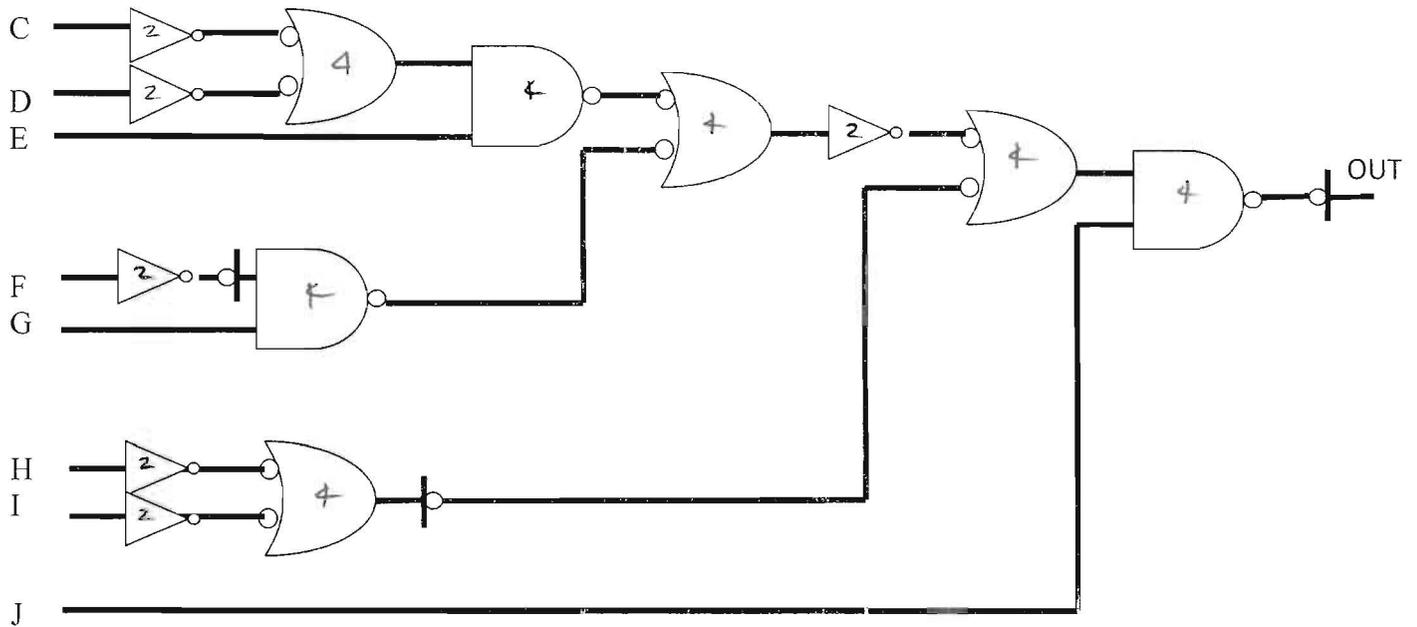3) Part A (15 points) Write the boolean output expression for the gate design shown below. Also determine the number of switches used in its implementation.





Out 
$$\left( \left( \left( (C+D) \cdot E \right) + \bar{F} \cdot G \right) + \overline{(H+I)} \right) J = (C+D)E + \bar{F}G + \overline{H+I} \right) J$$

number of switches 40

$$6 \times 2 + 7 \times 4 = 40$$

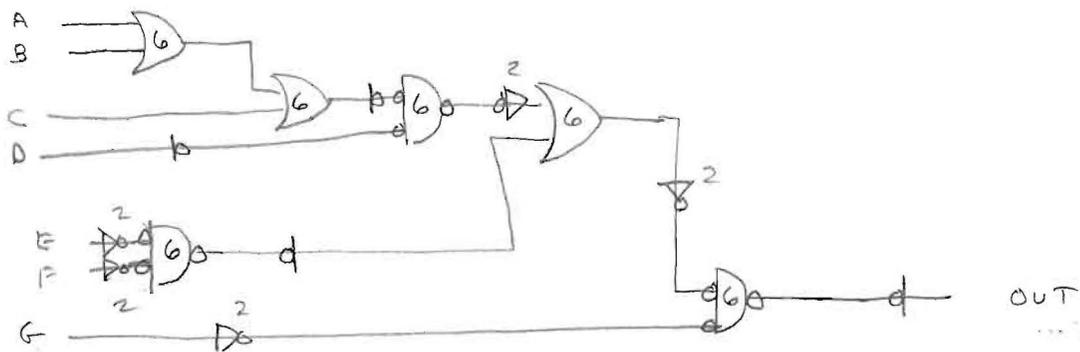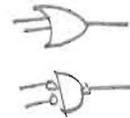3) Part B (15 points) Implement the following expression using only two input OR gates and inverters so as to minimize the number of switches required. Then determine the number of switches required. **Use proper mixed logic notation.** Do not modify the expression, do not simplify the expression. Do not assume complements of inputs are available. 6

$$\text{Out} = \overline{((A + B + C) \cdot \bar{D} + \overline{EF}) \cdot G}$$




Number of switches 46

$$6 \times 6 + 5 \cdot 2 = 36 + 10 = 46$$

Karnaugh Maps:

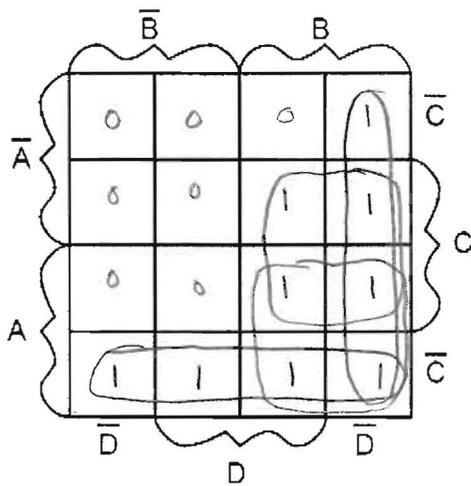4) (15 points) For the following expression, derive a simplified *sum of products* expression using a Karnaugh Map. Circle and list **ALL** the prime implicants, indicating which are essential.

$$A \cdot \bar{C} + A \cdot B \cdot \bar{C} + B \cdot \bar{D} + B \cdot C \cdot D$$



| prime implicants  | essential?                          |                                     |
|-------------------|-------------------------------------|-------------------------------------|
|                   | yes                                 | no                                  |
| $A \cdot \bar{C}$ | <input checked="" type="checkbox"/> | <input type="checkbox"/>            |
| $B \cdot \bar{D}$ | <input type="checkbox"/>            | <input checked="" type="checkbox"/> |
| $B \cdot C$       | <input checked="" type="checkbox"/> | <input type="checkbox"/>            |
| $A \cdot B$       | <input type="checkbox"/>            | <input checked="" type="checkbox"/> |
|                   | <input type="checkbox"/>            | <input type="checkbox"/>            |
|                   | <input type="checkbox"/>            | <input checked="" type="checkbox"/> |
|                   | <input type="checkbox"/>            | <input type="checkbox"/>            |
|                   | <input type="checkbox"/>            | <input type="checkbox"/>            |

Simplified sum of products  $A \cdot \bar{C} + B \cdot C + B \cdot \bar{D}$

5) (10 points) Determine the canonical product of sums (using maxterms) expressions for the truth table below:


| A | B | C | OUT |
|---|---|---|-----|
| 0 | 0 | 0 | 1   |
| 0 | 0 | 1 | 1   |
| 0 | 1 | 0 | 1   |
| 0 | 1 | 1 | 1   |
| 1 | 0 | 0 | 0   |
| 1 | 0 | 1 | 0   |
| 1 | 1 | 0 | 0   |
| 1 | 1 | 1 | 0   |

$\bar{A} + B + C$   
 $\bar{A} + B + \bar{C}$   
 $\bar{A} + \bar{B} + C$   
 $\bar{A} + \bar{B} + \bar{C}$

POS (maxterms) =  $(\bar{A} + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)(\bar{A} + \bar{B} + \bar{C})$

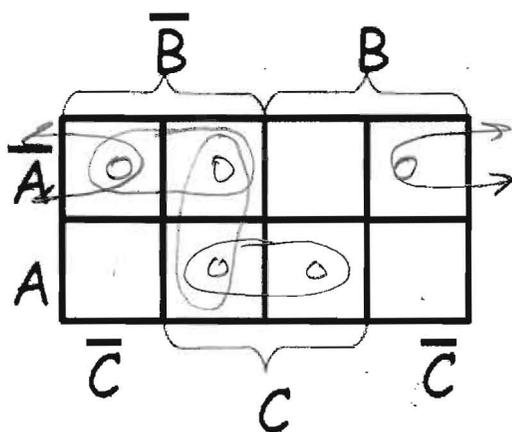6) (15 points) For the following expression, derive a simplified **product of sums** expression using a Karnaugh Map. Circle and list **ALL** the prime implicants, indicating which are essential.

out =  $(A+B+C)(A+\bar{B}+C)(A+B+\bar{C})(\bar{A} + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})$



| prime implicants    | essential?                          |                                     |
|---------------------|-------------------------------------|-------------------------------------|
|                     | yes                                 | no                                  |
| $\bar{A} + \bar{C}$ | <input checked="" type="checkbox"/> | <input type="checkbox"/>            |
| $A + C$             | <input checked="" type="checkbox"/> | <input type="checkbox"/>            |
| $B + \bar{C}$       | <input type="checkbox"/>            | <input checked="" type="checkbox"/> |
| $A + B$             | <input type="checkbox"/>            | <input checked="" type="checkbox"/> |
|                     | <input type="checkbox"/>            | <input type="checkbox"/>            |

Simplified product of sums =  $(\bar{A} + \bar{C})(A + C)(B + \bar{C})$

$(\bar{A} + \bar{C})(A + C)(A + B)$